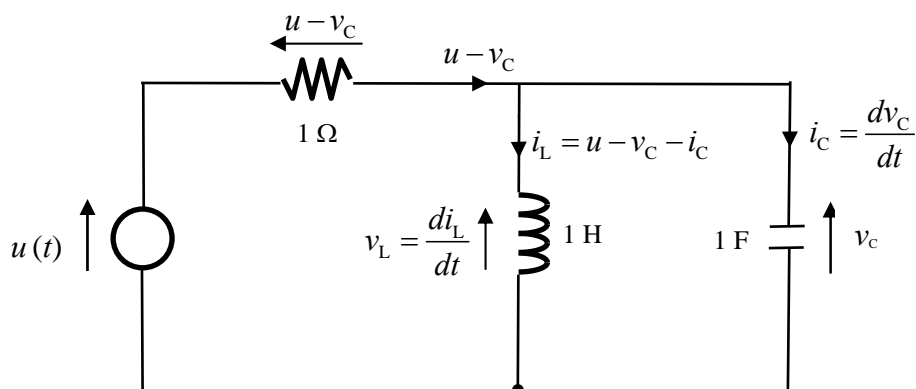


Q.1. In the electrical circuit given below, $u(t) = 10 \text{ V}$, and both the capacitor and inductor are initially discharged.



(a) Show the differential equation governing the circuit in terms of v_c is given as

$$\frac{d^2 v_c(t)}{dt^2} + \frac{dv_c(t)}{dt} + v_c(t) = \frac{du(t)}{dt}$$

Give all the detailed derivations in obtaining the above differential equation.

(10 marks)

Solution: From all the currents and voltages labeled in the circuit above, we have

$$v_c = v_L = \frac{di_L}{dt} = \frac{d}{dt}(u - v_c - i_c) = \frac{d}{dt}\left(u - v_c - \frac{dv_c}{dt}\right) = \frac{du}{dt} - \frac{dv_c}{dt} - \frac{d^2 v_c}{dt^2}$$

$$\Downarrow$$

$$\frac{d^2 v_c}{dt^2} + \frac{dv_c}{dt} + v_c = \frac{du}{dt}$$

(b) Compute the roots of the characteristic polynomial of the circuit.

(5 marks)

Solution: The characteristic polynomial is given by

$$z^2 + z + 1 = 0 \Rightarrow z_1, z_2 = -\frac{1}{2} \pm j \frac{\sqrt{3}}{2} = -0.5 \pm j0.866$$

(c) Determine the steady-state values of i_L , i_C and v_C .

(5 marks)

Solution: $i_L(\infty) = 10$, $i_C(\infty) = 0$, $v_C(\infty) = 0$

(d) Determine the complete solution of $v_C(t)$.

(5 marks)

Solution: The complete solution is given by

$$v_C(t) = v_{C,ss} + v_{C,tr} = 0 + k_1 e^{z_1 t} + k_2 e^{z_2 t} = k_1 e^{(-0.5 + j0.866)t} + k_2 e^{(-0.5 - j0.866)t}$$

Since the capacitor is initially discharged, we have

$$v_C(0) = k_1 + k_2 = 0$$

Also,

$$\begin{aligned} i_L &= u - v_C - \frac{dv_C}{dt} \\ &= 10 - k_1 e^{(-0.5 + j0.866)t} - k_2 e^{(-0.5 - j0.866)t} - (-0.5 + j0.866)k_1 e^{(-0.5 + j0.866)t} - (-0.5 - j0.866)k_2 e^{(-0.5 - j0.866)t} \end{aligned}$$

The condition that the inductor is initially discharged implies

$$\begin{aligned} i_L(0) &= 10 - k_1 - k_2 - (-0.5 + j0.866)k_1 - (-0.5 - j0.866)k_2 \\ &= 10 - j0.866(k_1 - k_2) = 0 \\ &\Downarrow \\ k_2 - k_1 &= j11.5473 \quad \Rightarrow \quad k_1 = -j5.7737, \quad k_2 = j5.7737 \end{aligned}$$


Hence,

$$v_C(t) = -j5.7737 e^{(-0.5 + j0.866)t} + j5.7737 e^{(-0.5 - j0.866)t} = 11.5473 e^{-0.5t} \sin 0.866t$$

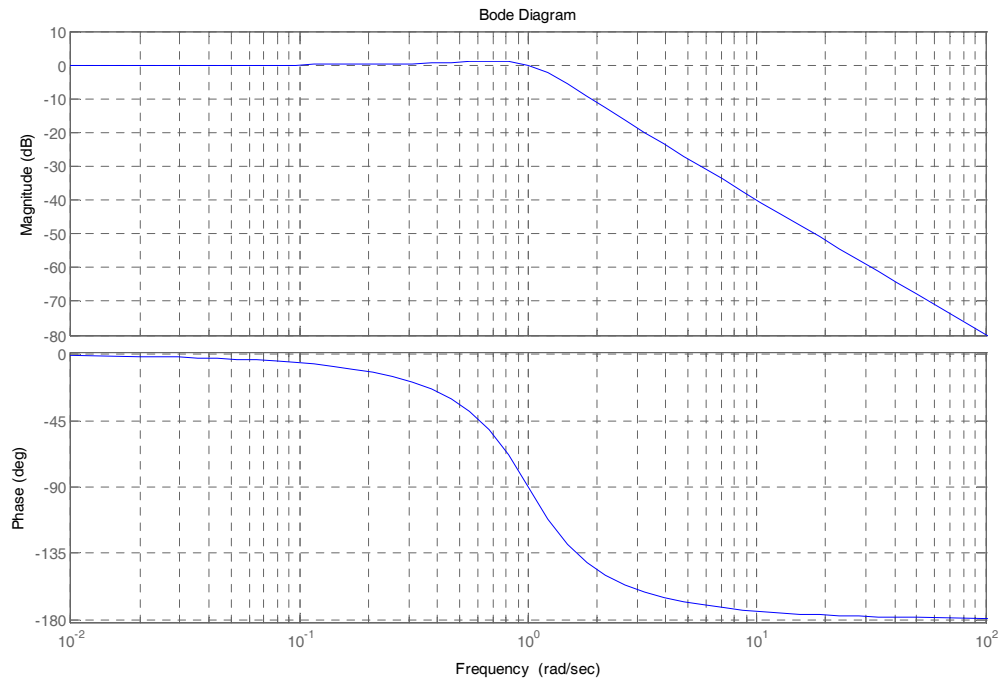Q.2. It can be shown that the electric system given in Q.1 has a transfer function from the inductor current i_L to the input voltage source u is given by

$$H(s) = \frac{I_L(s)}{U(s)} = \frac{1}{s^2 + s + 1}$$

and its Bode plot is given as in the figure below.



- (a) Find the DC gain, K , the damping ratio, ζ , and the natural frequency, ω_n , of the given system.

(5 marks)

Solution: Observing that

$$H(s) = \frac{I_L(s)}{U(s)} = \frac{1}{s^2 + s + 1} = \frac{K\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} \Rightarrow K=1, \omega_n=1, \zeta=0.5$$

(b) Given an input, $u(t) = \cos t$, find its corresponding steady-state output, $i_L(t)$.

(5 marks)

Solution: $i_L(t) = \cos(t - 90^\circ)$

(c) Given an input, $u(t) = \cos 100 t$, find its corresponding steady-state output, $i_L(t)$.

(5 marks)

Solution: $i_L(t) = 10^{-4} \cos(100t - 180^\circ)$

(d) Sketch the unit step response.

(10 marks)

Solution:

