

Q.3 (a) Prove the following De Morgan's law:

$$\overline{A+B+C} = \overline{A} \cdot \overline{B} \cdot \overline{C}$$

(5 Marks)

Give your answer to Q.3(a) in the space below.

Proof. This can be done by using truth tables as follows:

A	B	C	$\overline{A+B+C}$	$\overline{A} \cdot \overline{B} \cdot \overline{C}$
0	0	0	1	1
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0

The result is obvious.

Q.3 (b) Use the De Morgan's laws and any of first 17 rules of Boolean Algebra to prove the last rule, i.e., Rule 18:

$$A + \overline{A} \cdot B = A + B$$

(5 Marks)

Give your answer to Q.3(b) in the space below.

Proof.

$$A + \overline{A} \cdot B = \overline{\overline{A + \overline{A} \cdot B}} = \overline{\overline{A} \cdot \overline{\overline{A} \cdot B}} = \overline{\overline{A} \cdot (A + B)} = \overline{\overline{A} \cdot A + \overline{A} \cdot B} = \overline{\overline{A} \cdot B} = A + B$$

or any other correct forms.

Q.3 (c) Consider a logical expression

$$W = (\overline{A + \overline{C}}) \cdot (B + C)$$

- (i) Construct a truth table for W . (5 Marks)
- (ii) Use the Karnaugh map technique to simplify the logical expression. (5 Marks)
- (iii) Implement the logical expression obtained in (ii) using only 2 two-input NOR gates. (5 Marks)

Give your answer to Q.3(c) in the space below. If necessary, continue on the next page.

Solution. (i) The truth table:


A	B	C	$A + \overline{C}$	$\overline{A + \overline{C}}$	$B + C$	W
0	0	0	1	0	0	0
0	0	1	0	1	1	1
0	1	0	1	0	1	0
0	1	1	0	1	1	1
1	0	0	1	0	0	0
1	0	1	1	0	1	0
1	1	0	1	0	1	0
1	1	1	1	0	1	0

(ii) The K-map:

	$A \cdot B$	$A \cdot \overline{B}$	$\overline{A} \cdot \overline{B}$	$\overline{A} \cdot B$
C	0	0	1	1
\overline{C}	0	0	0	0

Clearly, we have $W = \overline{A} \cdot C$.

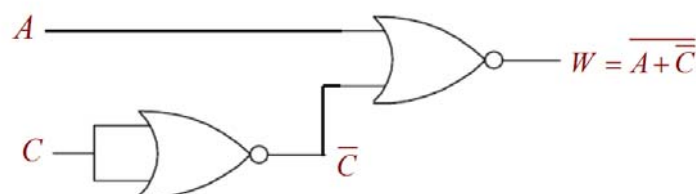(iii) Logic circuit implementation: $W = \overline{\overline{\overline{A} \cdot C}} = \overline{A + \overline{C}}$



- Q.4 (a)** Consider the transformer circuit shown in Figure Q4 (a) below. The transformer turns ratio is 1:2. The input to the circuit is the voltage source, $v_s(t)$. Determine the output voltage, $v_o(t)$, across the 2 H inductor.

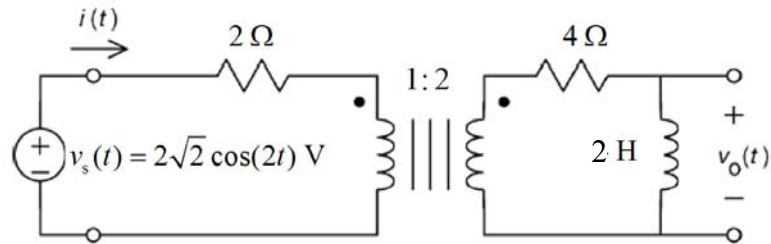


Figure Q4 (a)


(10 Marks)

Give your answer to Q.4(a) in the space below. If necessary, continue on the next page.

Solution. $\omega = 2$. Thus, the total load impedance of the circuit is given by

$$Z_L = 4 + j2 \times 2 = 4 \times (1 + j)$$

The circuit is equivalent to

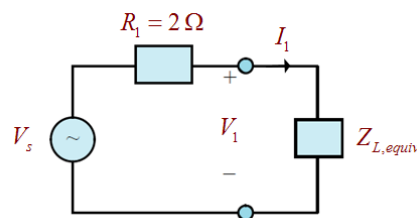

with $Z_{L,equiv} = \frac{Z_L}{n^2} = \frac{4 \times (1 + j)}{2^2} = 1 + j$ and $V_s = 2$. Thus, we have

$$I_1 = \frac{V_s}{2 + (1 + j)} = \frac{2}{3 + j} = \frac{2(3 - j)}{(3 + j)(3 - j)} = \frac{3 - j}{5}$$

$$I_2 = \frac{I_1}{n} = \frac{3 - j}{10}$$

$$V_o = I_2 \cdot (j4) = \frac{3 - j}{10} \cdot (j4) = \frac{2}{5}(1 + j3) = \frac{2\sqrt{10}}{5} \angle \tan^{-1} 3$$

Thus,

$$v_o(t) = \frac{2\sqrt{10}}{5} \sqrt{2} \cos(2t + \tan^{-1} 3) = \frac{4\sqrt{5}}{5} \cos(2t + \tan^{-1} 3) = 1.8 \cos(2t + 71.6^\circ)$$


Q.4 (b) A DC power supply consists of a transformer feeding a half-wave rectifier together with a capacitor filter. It supplies a DC current of 1 A at 20 V DC to an electronic equipment. The AC input source is 230 V (rms) at 50 Hz. The filter capacitor has a capacitance of 60,000 μ F.

- (i) Draw the circuit diagram of the supply arrangement. (5 Marks)
- (ii) Determine a suitable winding ratio for the transformer. (5 Marks)
- (iii) Determine the magnitude of the peak-to-peak ripple in the output voltage. (5 Marks)

Give your answer to Q.4(b) in the space below. If necessary, continue on the next page.

Solution.

(i)

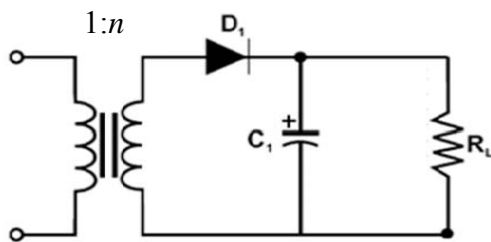

(ii) $V_{ave} \cong V_m = 20$.

$$n = \frac{V_2}{V_1} = \frac{V_m / \sqrt{2}}{230} = \frac{20}{230\sqrt{2}} = \frac{\sqrt{2}}{23} = 0.0615$$

(iii)

$$V_{p-p} = \frac{I_L T}{C_1} = \frac{I_L}{C_1 f} = \frac{1}{60000 \times 10^{-6} \times 50} = \frac{1}{3} \text{ V}$$