
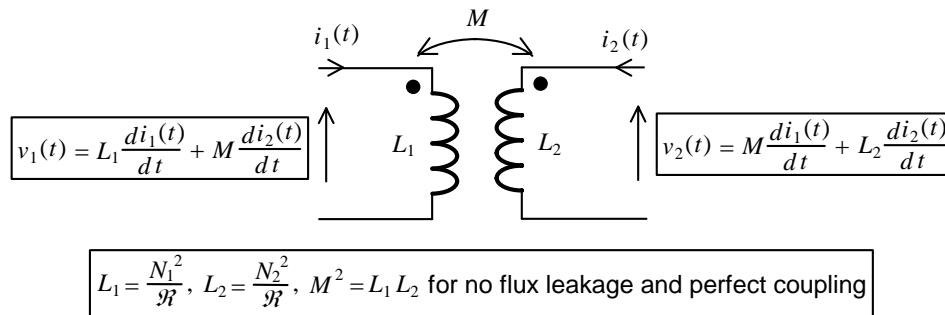


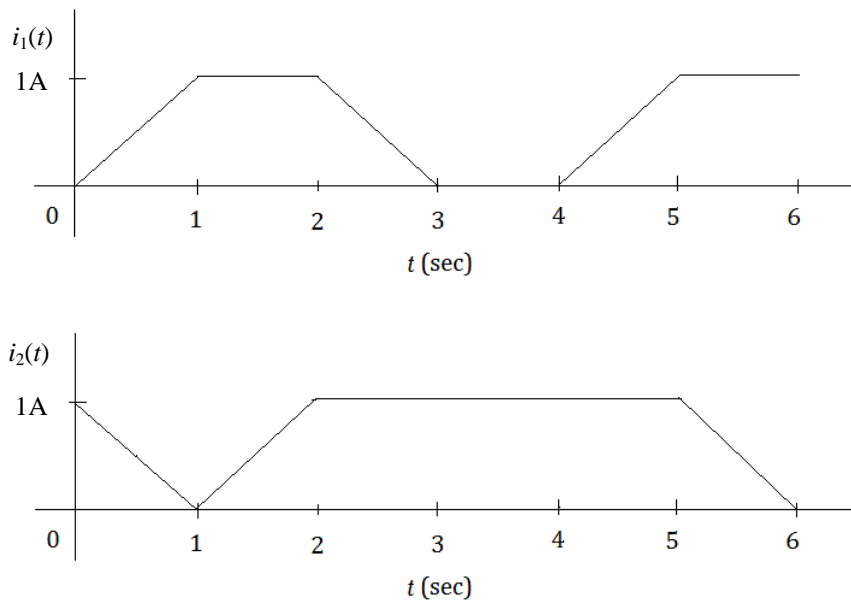Q.3 Shown in the figure below is the expressions of the primary and secondary voltages of an ideal transformer. Assume that the transformer reluctance $\mathfrak{R} = 25$, the numbers of the turns of the primary and secondary windings are $N_1 = 10$, $N_2 = 5$, respectively.



(a) Given the waveforms of $i_1(t)$ and $i_2(t)$ as the figure below,



sketch the waveforms of the induced voltages, $v_1(t)$ and $v_2(t)$.





(10 Marks)

Solution:


$$L_1 = \frac{N_1^2}{\mathfrak{R}} = \frac{100}{25} = 4, \quad L_2 = \frac{N_2^2}{\mathfrak{R}} = \frac{25}{25} = 1, \quad M = \sqrt{L_1 L_2} = 2$$

$$v_1(t) = 4 \frac{di_1(t)}{dt} + 2 \frac{di_2(t)}{dt}, \quad v_2(t) = 2 \frac{di_1(t)}{dt} + \frac{di_2(t)}{dt}$$

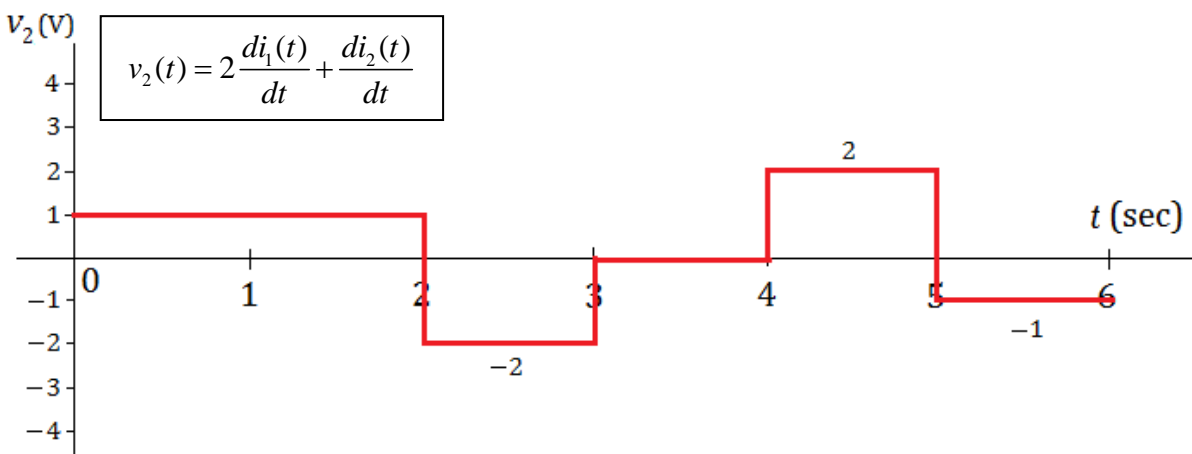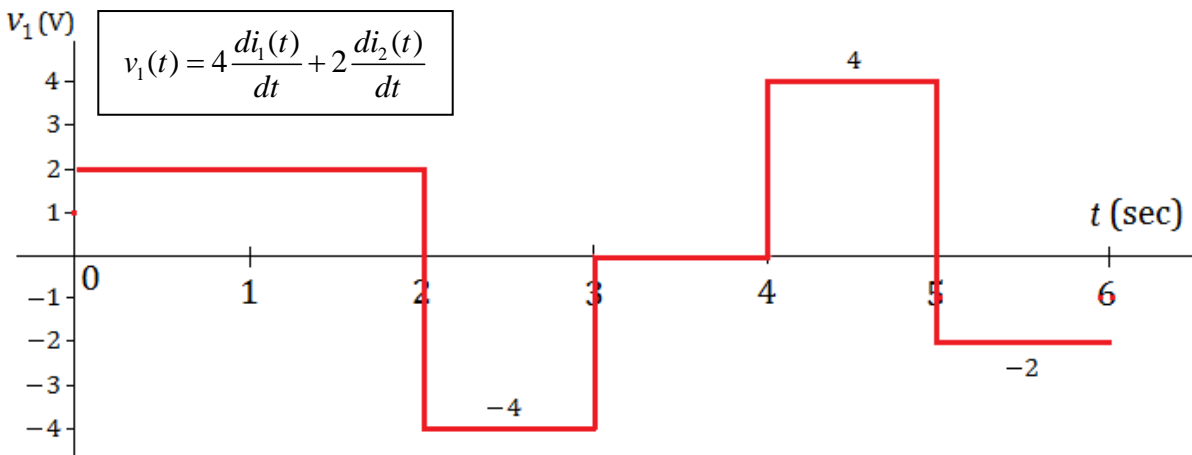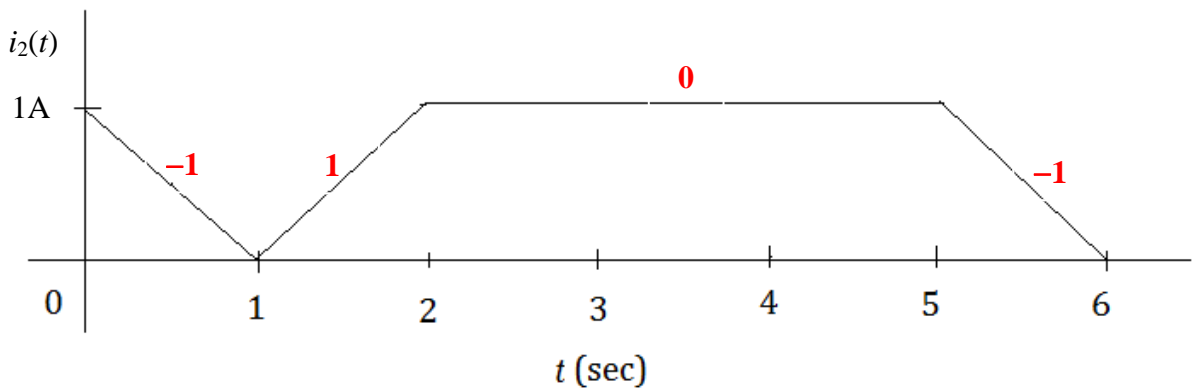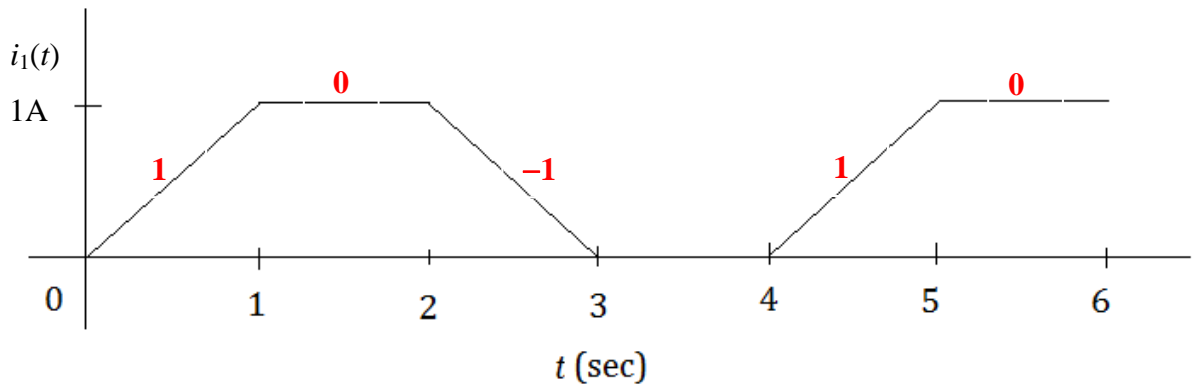Sketch the waveforms directly on the graphs below.



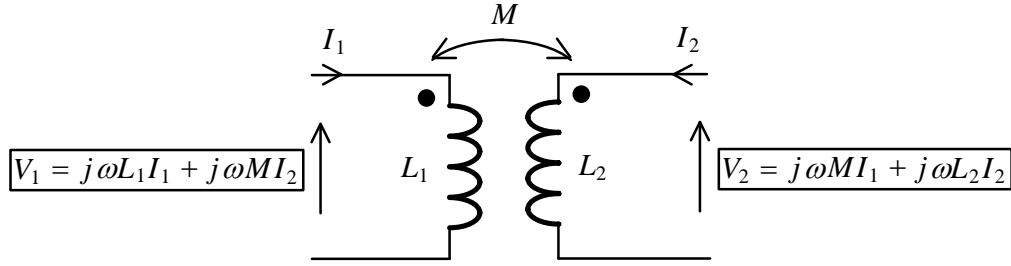- (b) For AC environments, show that the primary and secondary voltages in the phasor form are given as those in the figure below.



Hint: Assume $i_1(t) = \sqrt{2} r_1 \cos(\omega t + \theta_1)$ and $i_2(t) = \sqrt{2} r_2 \cos(\omega t + \theta_2)$.

(5 Marks)

Proof:

$$i_1(t) = \sqrt{2} r_1 \cos(\omega t + \theta_1) \Rightarrow I_1 = r_1 e^{j\theta_1}, \quad i_2(t) = \sqrt{2} r_2 \cos(\omega t + \theta_2) \Rightarrow I_2 = r_2 e^{j\theta_2}$$


$$\begin{aligned} v_1(t) &= L_1 \frac{di_1(t)}{dt} + M \frac{di_2(t)}{dt} = -L_1 \sqrt{2} r_1 \omega \sin(\omega t + \theta_1) - M \sqrt{2} r_2 \omega \sin(\omega t + \theta_2) \\ &= L_1 \sqrt{2} r_1 \omega \cos(\omega t + \theta_1 + 90^\circ) + M \sqrt{2} r_2 \omega \cos(\omega t + \theta_2 + 90^\circ) \end{aligned}$$

$$V_1 = \omega L_1 r_1 e^{j(\theta_1 + 90^\circ)} + \omega M r_2 e^{j(\theta_2 + 90^\circ)} = j\omega L_1 r_1 e^{j\theta_1} + j\omega M r_2 e^{j\theta_2} = j\omega L_1 I_1 + j\omega M I_2$$

$$\begin{aligned} v_2(t) &= M \frac{di_1(t)}{dt} + L_2 \frac{di_2(t)}{dt} = -M \sqrt{2} r_1 \omega \sin(\omega t + \theta_1) - L_2 \sqrt{2} r_2 \omega \sin(\omega t + \theta_2) \\ &= M \sqrt{2} r_1 \omega \cos(\omega t + \theta_1 + 90^\circ) + L_2 \sqrt{2} r_2 \omega \cos(\omega t + \theta_2 + 90^\circ) \end{aligned}$$

$$V_2 = \omega M r_1 e^{j(\theta_1 + 90^\circ)} + \omega L_2 r_2 e^{j(\theta_2 + 90^\circ)} = j\omega M r_1 e^{j\theta_1} + j\omega L_2 r_2 e^{j\theta_2} = j\omega M I_1 + j\omega L_2 I_2$$

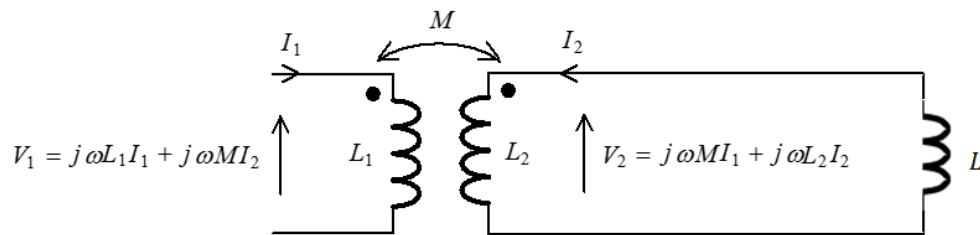- (c) The transformer is connected to a load inductor with inductance $L = 2 \text{ H}$, as shown in the figure below. Recall that the transformer reluctance $\mathfrak{R} = 25$, the numbers of the turns of the primary and secondary windings are $N_1 = 10$, $N_2 = 5$, respectively. Determine the ratio of the primary and secondary currents (in phasor).



Why is the usual transformer property below no longer valid in such a situation?

$$\frac{I_1}{I_2} = -\frac{N_2}{N_1}$$

(10 Marks)

Solution:

$$Z_L = j\omega L = j2\omega$$

$$V_2 = j2\omega I_1 + j\omega I_2$$

By KVL,

$$V_2 + I_2 Z_L = j2\omega I_1 + j\omega I_2 + j2\omega I_2 = j2\omega I_1 + j3\omega I_2 = 0$$


\Downarrow

$$2I_1 + 3I_2 = 0$$

$$\frac{I_1}{I_2} = -\frac{3}{2} \neq -\frac{N_2}{N_1} = -\frac{1}{2}$$

This is because $|Z_L| = |j2\omega| = 2\omega > |j\omega L_2| = |j\omega| = \omega$. The condition $|j\omega L_2| \gg |Z_L|$ is invalid.

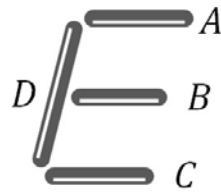Q.4 An LED display panel shown in the figure below has four LED light bars labeled *A*, *B*, *C* and *D*, respectively. You are required to design an appropriate digital logic circuit to display Letters *F* and *L* using the panel.



- (a) Construct a truth table for your design. (6 Marks)
- (b) Obtain logical expressions for *F* and *L*, respectively. (6 Marks)
- (c) Draw logic circuit implementations for *F* and *L* using only 2-input NOR gates (i.e., each NOR gate only has two input channels). For each letter, you cannot use more than 8 NOR gates for the implementation. (10 Marks)
- (d) What other English letters can be displayed by the panel? (3 Marks)

Solution to Q4 (a):

	<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>	<i>L</i>
0	0	0	0	0	0	0
1	0	0	0	1	0	0
2	0	0	1	0	0	0
3	0	0	1	1	0	1
4	0	1	0	0	0	0
5	0	1	0	1	0	0
6	0	1	1	0	0	0
7	0	1	1	1	0	0
8	1	0	0	0	0	0
9	1	0	0	1	0	0
10	1	0	1	0	0	0
11	1	0	1	1	0	0
12	1	1	0	0	0	0
13	1	1	0	1	1	0
14	1	1	1	0	0	0
15	1	1	1	1	0	0

(6 Marks)


Solution to Q4 (b):

$$F = A \cdot B \cdot \bar{C} \cdot D, \quad L = \bar{A} \cdot \bar{B} \cdot C \cdot D$$

(6 Marks)


Solution to Q4 (c):
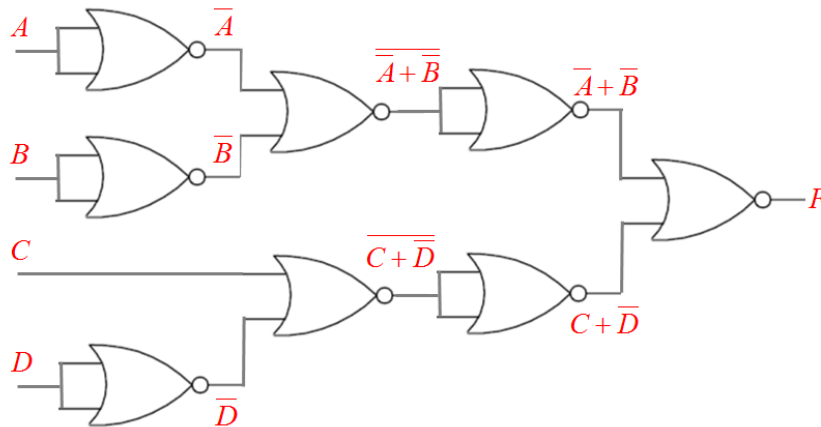
$$F = A \cdot B \cdot \bar{C} \cdot D = \overline{\overline{A \cdot B \cdot \bar{C} \cdot D}} = \overline{\overline{(A+B)} + \overline{(C+D)}} = \overline{\overline{\overline{\overline{A+B}} + \overline{\overline{\overline{\overline{C+D}}}}}} = \overline{\overline{\overline{A+B} + \overline{\overline{\overline{C+D}}}}}$$



(5 Marks)
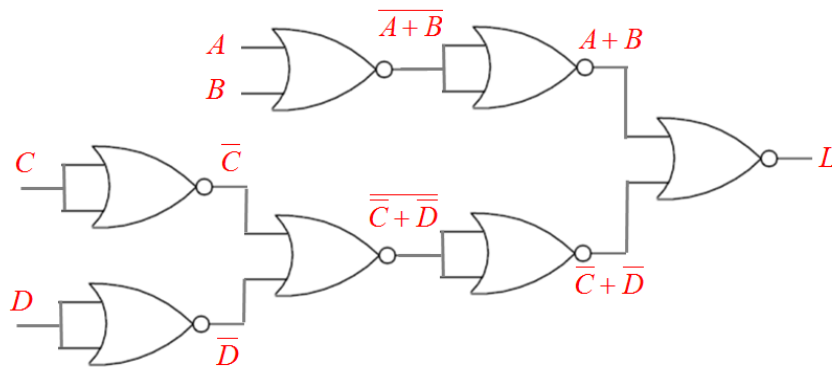
$$L = \bar{A} \cdot \bar{B} \cdot C \cdot D = \overline{\overline{\overline{\overline{\bar{A} \cdot \bar{B} \cdot C \cdot D}}}} = \overline{\overline{(A+B)} + \overline{(C+D)}} = \overline{\overline{\overline{\overline{A+B}} + \overline{\overline{\overline{\overline{C+D}}}}}} = \overline{\overline{\overline{A+B} + \overline{\overline{\overline{C+D}}}}}$$



(5 Marks)

Solution to Q4 (d):

Letters, **C**, **E** and **I**.

(3 Marks)