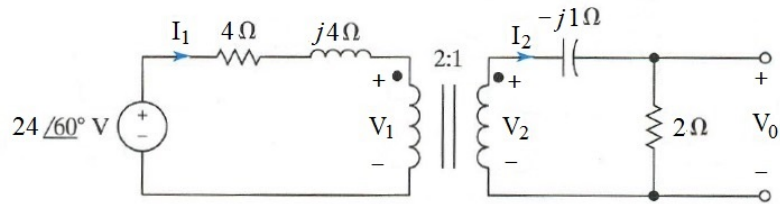


Q.3 Shown in the figure below is a transformer circuit.




(a) Find V_0 in the phasor form.

(10 Marks)

Solution: Using the equivalent load of the transformer circuit, we can convert the given circuit into the following form with an equivalent load

$$Z_{\text{equivload}} = \frac{2-j}{\left(\frac{1}{2}\right)^2} = 8-j4$$

or

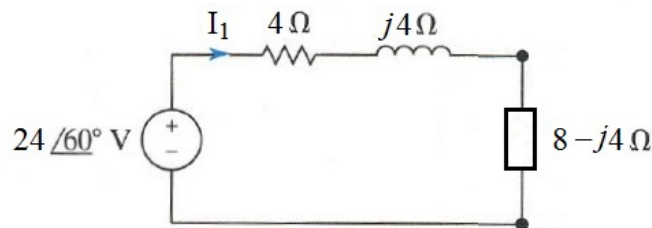

$$I_1 = \frac{24\angle 60^\circ}{4 + j4 + 8 - j4} = \frac{24\angle 60^\circ}{12} = 2\angle 60^\circ$$

$$I_2 = \frac{I_1}{n} = \frac{2\angle 60^\circ}{\frac{1}{2}} = 4\angle 60^\circ$$

$$V_0 = 2 I_2 = 8\angle 60^\circ \text{ V}$$

- (b) Given the frequency of the AC source $f = 50$ Hz, find the corresponding time domain function of the output, $v_0(t)$.

(5 Marks)

Solution: Ideal transformers do not consume power.

$$v_0(t) = 8\sqrt{2} \cos(\omega t + 60^\circ) = 8\sqrt{2} \cos(2\pi f t + 60^\circ) = 11.3137 \cos(314 t + 60^\circ) \text{ V}$$

- (c) Can the output voltage $v_0(t)$ be connected to a rectified circuit to produce a constant DC output voltage of 30 V? If the answer is no, suggest a solution to the problem.

(10 Marks)

Solution: The maximum constant DC voltage that a rectified circuit can produce is the peak value of the AC input, which is 11.3137 V.

Thus, the output voltage $v_0(t)$ cannot be connected to a rectified circuit to produce a constant DC output voltage of 30 V.

Another transformer is needed to step up 11.3137 V to 30 V in order to produce a 30 V DC output.

Q.4 A long hallway has three doors, one at each end and one in the middle. Each door side has a switch to control the hallway's light. The light is off when switch variables, S_1 , S_2 and S_3 , have the values 0, 0 and 0. Otherwise, the light is on. Design a combinational network that controls the light (L).

- (a) Follow the format set in the lecture notes to construct a truth table with inputs S_1 , S_2 and S_3 , and output L . No credit to be awarded if the truth table does not follow the standard format.

(10 Marks)

Solution: The truth table

	S_1	S_2	S_3	L
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	1
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1


- (b) Obtain the logical expression for L in the POS form with all the maxterms.

(5 Marks)

Solution: The truth table

$$L = S_1 + S_2 + S_3$$

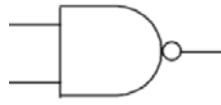- (c) Draw a logic circuit realization for the logical expression obtained in Part (b) using no more than 6 two-input only NAND gates (i.e., each NAND gate has only two inputs):



(10 Marks)

Solution:

$$L = \overline{\overline{S_1 + S_2 + S_3}} = \overline{\overline{S_1} \cdot \overline{S_2} \cdot \overline{S_3}} = \overline{\overline{\overline{\overline{S_1} \cdot \overline{S_2} \cdot \overline{S_3}}}}$$

Logic circuit realization

