

Q.3 (a) Which one of the following truth tables is incorrect in accordance with the standard format given in the EG1108 lecture? Reconstruct the incorrect truth table in the standard format.

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

(i)

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

(ii)

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	1	0
1	1	0	1
1	0	0	0
1	1	1	1

(iii)

(5 marks)

Write your answer to Q.3(a) in the space below.

Solution: (iii) is incorrect. The correct form is

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- (b) Which one of the following Karnaugh maps is incorrect? Reconstruct the incorrect Karnaugh map in the standard format.

	$A \cdot B$	$A \cdot \bar{B}$	$\bar{A} \cdot \bar{B}$	$\bar{A} \cdot B$
$C \cdot \bar{D}$	0	0	0	0
$\bar{C} \cdot \bar{D}$	0	0	1	0
$C \cdot D$	0	0	0	0
$\bar{C} \cdot D$	0	0	0	0

(i)

	$A \cdot \bar{B}$	$\bar{A} \cdot \bar{B}$	$\bar{A} \cdot B$	$A \cdot B$
$C \cdot D$	0	0	0	0
$C \cdot \bar{D}$	0	0	1	0
$\bar{C} \cdot \bar{D}$	0	0	0	0
$\bar{C} \cdot D$	0	0	0	0

(ii)

	$\bar{A} \cdot \bar{B}$	$\bar{A} \cdot B$	$A \cdot B$	$A \cdot \bar{B}$
$C \cdot \bar{D}$	0	0	0	0
$\bar{C} \cdot \bar{D}$	0	0	1	0
$\bar{C} \cdot D$	0	0	0	0
$C \cdot D$	0	0	0	0

(iii)

(5 marks)

Write your answer to Q.3(b) in the space below.

Solution: (i) is incorrect. The correct form is

	$A \cdot B$	$A \cdot \bar{B}$	$\bar{A} \cdot \bar{B}$	$\bar{A} \cdot B$
$\bar{C} \cdot \bar{D}$	0	0	1	0
$C \cdot \bar{D}$	0	0	0	0
$C \cdot D$	0	0	0	0
$\bar{C} \cdot D$	0	0	0	0

- (c) Simplify the following logical expression using only the 18 basic rules of Boolean algebra:

$$F = A \cdot B \cdot C \cdot \bar{D} + A \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot \bar{C} + \bar{A} \cdot B \cdot \bar{D} + B \cdot \bar{C}$$

(5 marks)

Write your answer to Q.3(c) in the space below.

Solution:

$$\begin{aligned} F &= A \cdot B \cdot C \cdot \bar{D} + A \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot \bar{C} + \bar{A} \cdot B \cdot \bar{D} + B \cdot \bar{C} \\ &= (A \cdot C + \bar{A}) \cdot B \cdot \bar{D} + (A \cdot \bar{B} + \bar{A} + B) \cdot \bar{C} \\ &= (C + \bar{A}) \cdot B \cdot \bar{D} + (\bar{B} + \bar{A} + B) \cdot \bar{C} \\ &= \bar{A} \cdot B \cdot \bar{D} + C \cdot B \cdot \bar{D} + \bar{C} \\ &= \bar{A} \cdot B \cdot \bar{D} + B \cdot \bar{D} + \bar{C} \\ &= (\bar{A} + 1) \cdot B \cdot \bar{D} + \bar{C} \\ &= B \cdot \bar{D} + \bar{C} \end{aligned}$$

- (d) Simplify the following logical expression in the SOP form using the Karnaugh map simplification technique:

$$F = A \cdot B \cdot C + A \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot \bar{C} + \bar{A} \cdot B \cdot \bar{D} + B \cdot \bar{C}$$

(5 marks)

Write your answer to Q.3(d) in the space below.

Solution:

	$A \cdot B$	$A \cdot \bar{B}$	$\bar{A} \cdot \bar{B}$	$\bar{A} \cdot B$
$C \cdot D$	1·1	0	0	0
$C \cdot \bar{D}$	1·1·1	0	0	1·1
$\bar{C} \cdot \bar{D}$	1·1·1	1	1	1·1
$\bar{C} \cdot D$	1·1	1	1	1

$$F = \bar{C} + A \cdot B + B \cdot \bar{D}$$


- (e) Realize a two-input NAND gate using only NOR gates.

(5 marks)

Write your answer to Q.3(e) in the space below.

Solution: Exclusive NOR gate can be expressed as
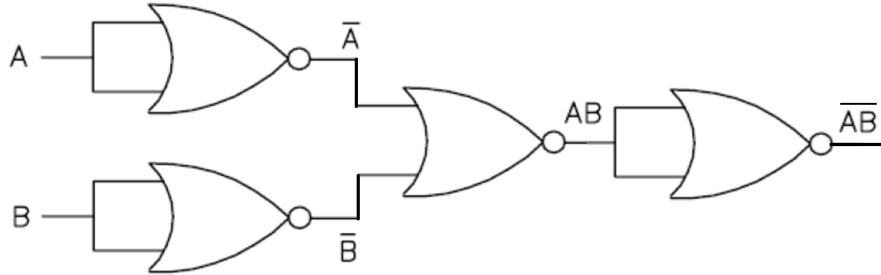
$$X = \overline{A \cdot B} = \overline{\overline{\overline{A + B}}}$$



Q.4 (a) Consider an ideal transformer circuit shown in Figure Q4 (a) below. The transformer turns ratio is 2:1. The input to the circuit is the voltage source, $v_s(t)$, as given in the circuit.


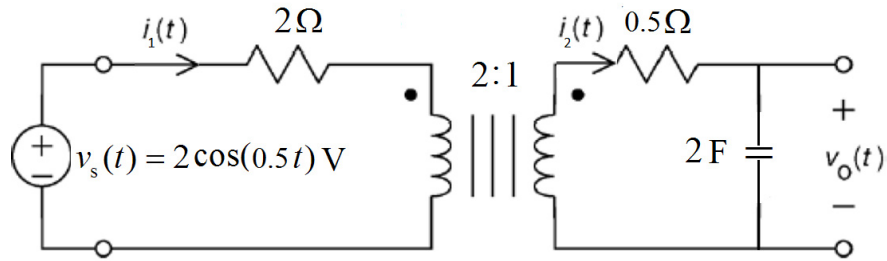
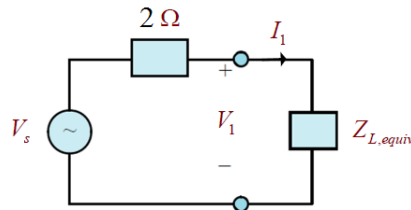


Figure Q4 (a)

- i) Determine the output voltage, $v_o(t)$, across the capacitor. (5 marks)
- ii) Determine the average power consumed by the capacitor and the transformer. (5 marks)

Solution: i)

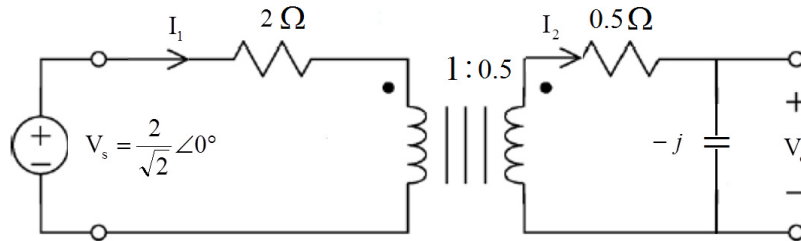

$$Z_{L,equiv} = \frac{0.5 - j}{0.5^2} = 2 - j4 \quad I_1 = \frac{V_s}{4 - j4} = \frac{2}{\sqrt{2}} \cdot \frac{1}{4\sqrt{2} \angle -45^\circ} = \frac{1}{4} \angle 45^\circ$$

$$I_2 = \frac{I_1}{0.5} = \frac{1}{2} \angle 45^\circ \Rightarrow V_o = -j \cdot I_2 = \frac{1}{2} \angle -45^\circ \Rightarrow v_o(t) = \frac{\sqrt{2}}{2} \cos(0.5t - 45^\circ)$$

- ii) Both the capacitor and the transformer do not consume any power.


Q.4 (b) A DC power supply consists of a transformer feeding a full-wave bridge rectifier with a capacitor filter. It supplies a DC current of 1 A at 5 V DC to a computer. The AC input source to the transformer is 230 V (rms) at 50 Hz. The filter capacitor has a capacitance of 0.05 F.

(i) Draw the circuit diagram of the supply arrangement. (5 marks)

(ii) Determine a suitable winding ratio for the transformer. (5 marks)

(iii) Determine the magnitude of the peak-to-peak ripple in the output voltage. (5 marks)

Solution: i)

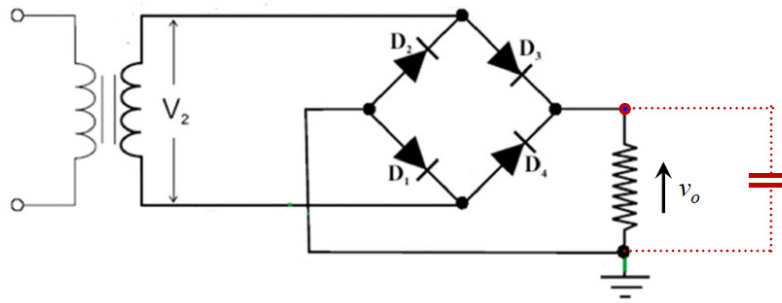

ii) The required turn ratio of the transformer:

$$\frac{1}{n} = \frac{230\sqrt{2}}{5} = 65 \quad \Rightarrow \quad 1:n = 65:1 = 1:0.0154$$

iii) The magnitude of the peak-to-peak ripple in the output voltage:

$$V_{p-p} = \frac{I_L T}{2R_L C} = \frac{I_L}{2fC} = \frac{1}{2 \times 50 \times 0.05} = 0.2 \text{ V}$$