
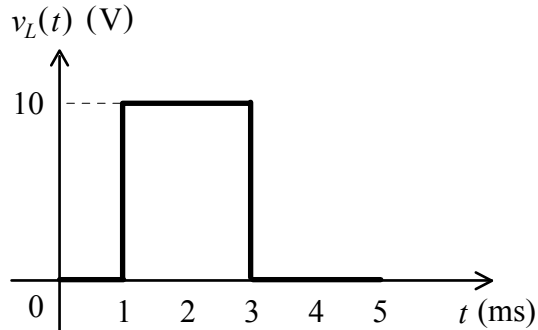
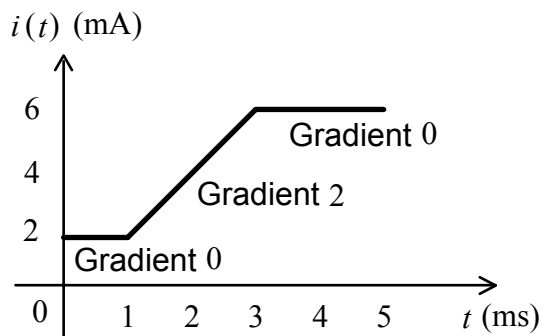



## Solution to Tutorial Set 2

Q.1

*Voltages across inductor*

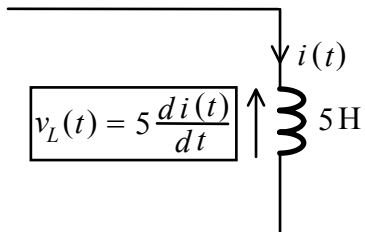

*Voltages across capacitor*

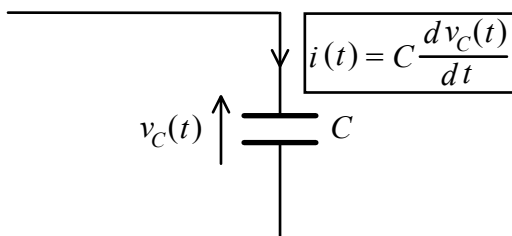


$$\int_0^t i(s) ds = \int_0^t C \frac{dv_C(s)}{ds} ds = \int_0^t C dv_C(s) = [Cv_C(s)]_0^t = C[v_C(t) - v_C(0)]$$

$$v_c(t) = v_c(0) + \frac{1}{C} \int_0^t i(s) ds$$

$$= [\text{initial voltage at } t=0] + \frac{1}{C} [\text{area under } i(t) \text{ from } 0 \text{ to } t]$$

For this problem:

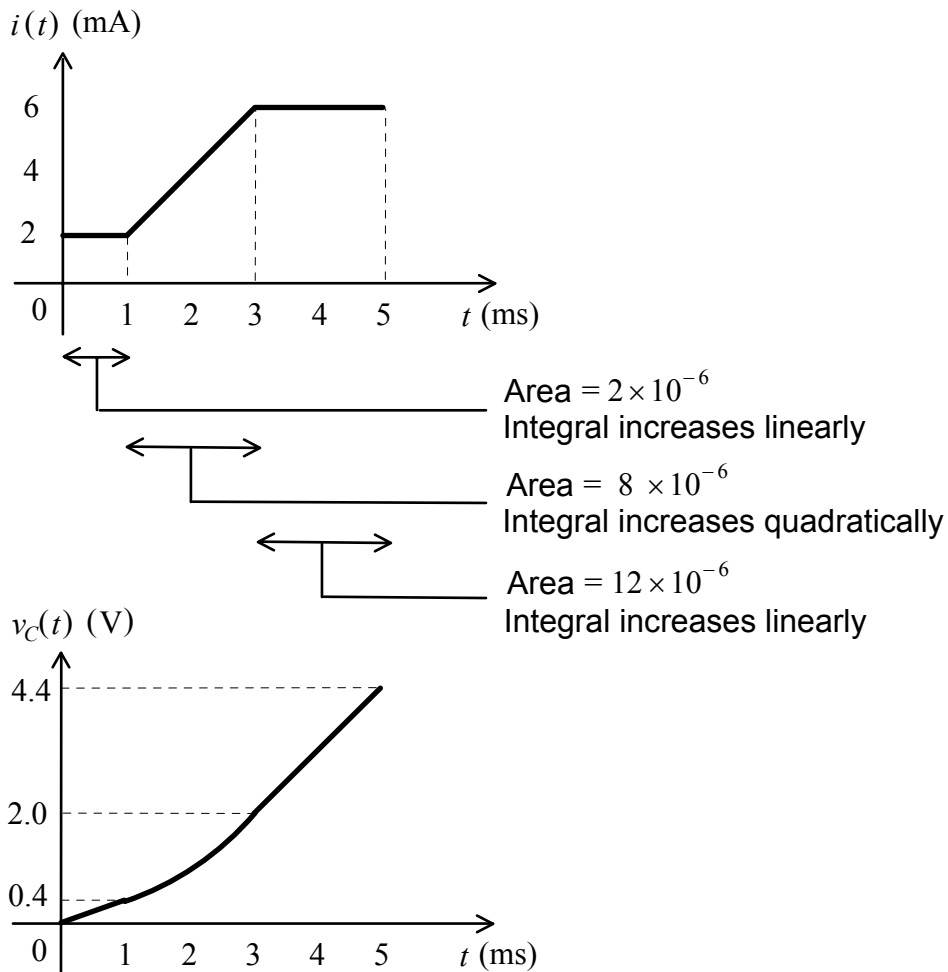
$$v_c(t) = \frac{1}{5 \times 10^{-6}} [\text{area under } i(t) \text{ from } 0 \text{ to } t]$$



Q.2



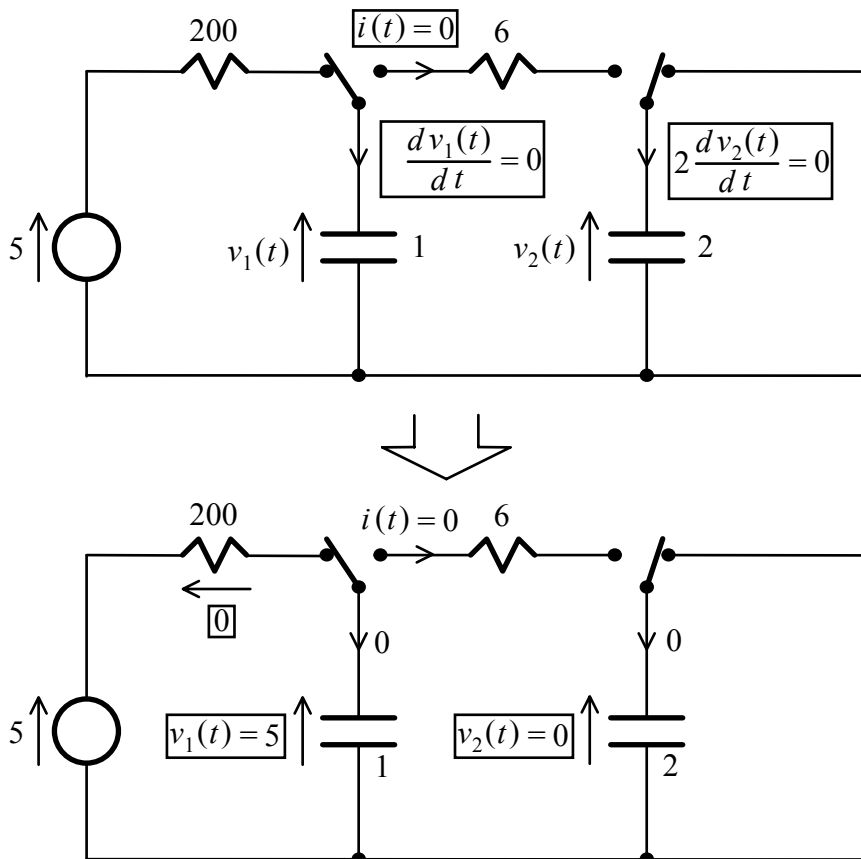
(a) Voltages and currents for  $t < 0$

With the source being a dc one and taking the switches to be in the positions shown starting from  $t = -\infty$ , all the voltages and currents will have settled down to constant values for practically all  $t < 0$ :




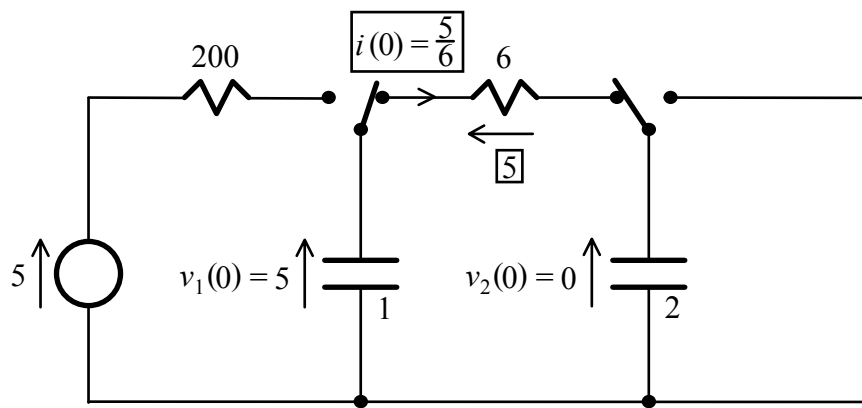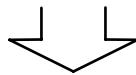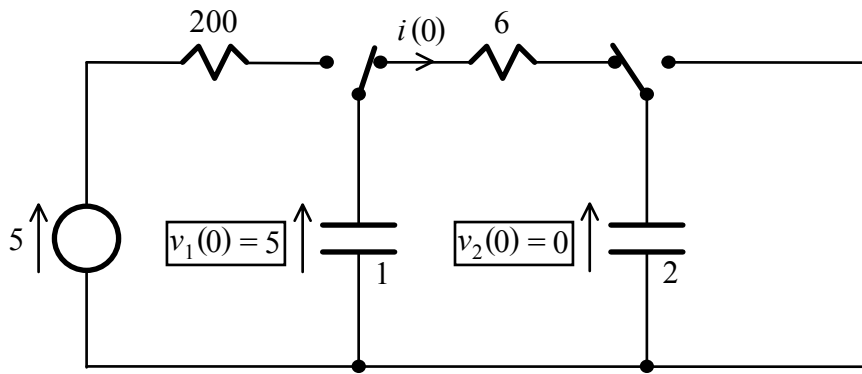(b) Voltages and currents at  $t = 0$  (just after the switches are thrown)

Since the voltages across capacitors must be continuous,  $v_1(0)$  and  $v_2(0)$  must have the same values before the switches are thrown:



(c) Voltages and current for  $t \geq 0$

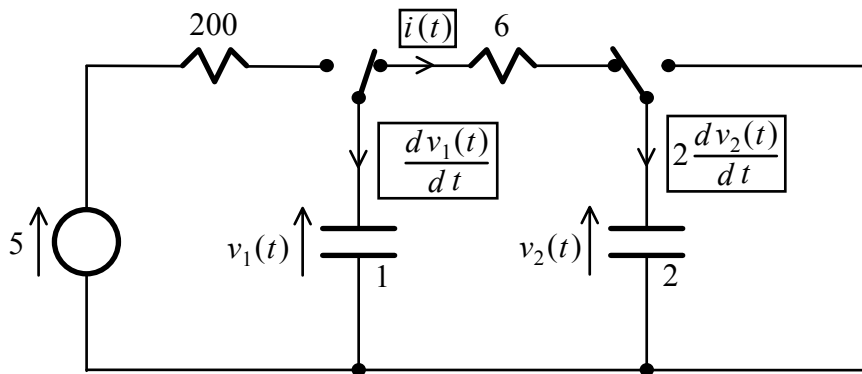

From KCL and KVL:

$$i(t) = 2 \frac{dv_2(t)}{dt} = - \frac{dv_1(t)}{dt}$$

$$v_1(t) - 6i(t) - v_2(t) = 0$$

Eliminating  $v_1(t)$  and  $v_2(t)$ :

$$\frac{dv_1(t)}{dt} - 6 \frac{di(t)}{dt} - \frac{dv_2(t)}{dt} = \left(-1 - \frac{1}{2}\right)i(t) - 6 \frac{di(t)}{dt} = 0 \Rightarrow \frac{di(t)}{dt} + \frac{i(t)}{4} = 0$$

Solving this homogeneous equation:

$$i(t) = ke^{-\frac{t}{4}}, t \geq 0$$

Applying initial condition:

$$i(0) = k = \frac{5}{6} \Rightarrow i(t) = \frac{5}{6}e^{-\frac{t}{4}}, t \geq 0$$


Solving for  $v_1(t)$  and  $v_2(t)$ :

$$\frac{dv_1(t)}{dt} = -i(t) = -\frac{5}{6}e^{-\frac{t}{4}} \Rightarrow v_1(t) = k_1 + \frac{10}{3}e^{-\frac{t}{4}}$$

$$v_1(0) = k_1 + \frac{10}{3} = 5 \Rightarrow k_1 = \frac{5}{3} \Rightarrow v_1(t) = \frac{5}{3} + \frac{10}{3}e^{-\frac{t}{4}}, t \geq 0$$

$$v_2(t) = v_1(t) - 6i(t) = \frac{5}{3} + \frac{10}{3}e^{-\frac{t}{4}} - 5e^{-\frac{t}{4}} = \frac{5}{3} - \frac{5}{3}e^{-\frac{t}{4}}, t \geq 0$$


(d) Voltages and current waveforms

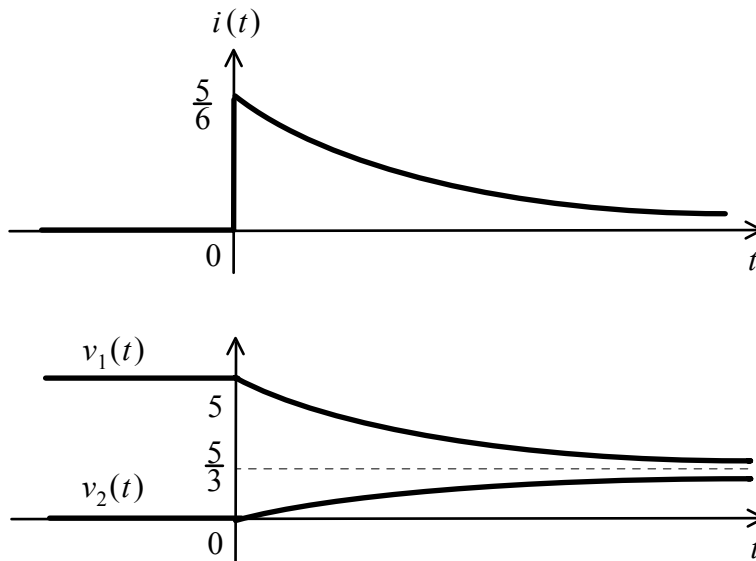

Q.3

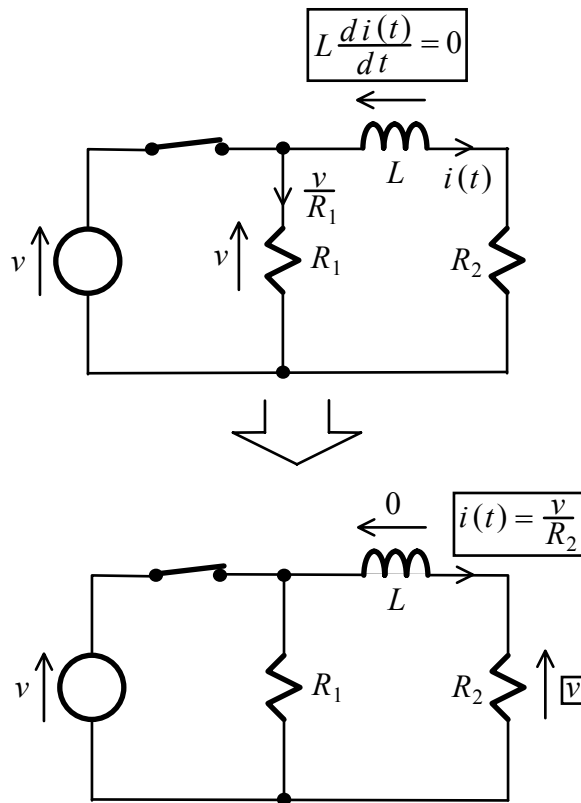(a) Voltages and current and energy stored for  $t < 0$


With the source being a dc one and taking the switches to be in the positions shown starting from  $t = -\infty$ , all the voltages and currents will have settled down to constant values for practically all  $t < 0$ :




$$\text{Energy stored in inductor} = \frac{Li^2(t)}{2} = \frac{Lv^2}{2R_2^2}$$

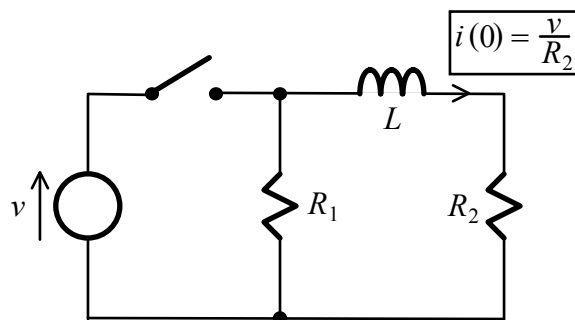(b) Current at  $t = 0$  (just after the switches is opened)

Since the current in the inductor must be continuous,  $i(0)$  must have the same value before the switch is opened:



(c) Current for  $t \geq 0$

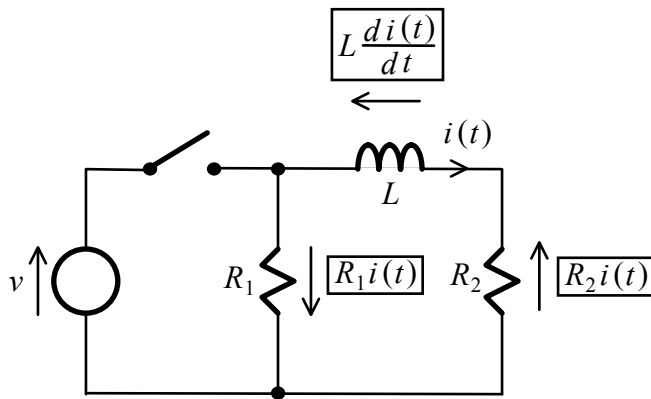

$$L \frac{di(t)}{dt} + R_1 i(t) + R_2 i(t) = 0 \Rightarrow \frac{di(t)}{dt} + \left( \frac{R_1 + R_2}{L} \right) i(t) = 0$$

$$i(t) = k e^{-\left( \frac{R_1 + R_2}{L} \right) t}, t \geq 0$$

$$i(0) = k = \frac{v}{R_2} \Rightarrow i(t) = \frac{v}{R_2} e^{-\left( \frac{R_1 + R_2}{L} \right) t}, t \geq 0$$

(d) Energy lost for  $t \geq 0$

$$\text{Instantaneous power lost in resistors} = (R_1 + R_2) i^2(t) = \frac{v^2 (R_1 + R_2)}{R_2^2} e^{-2 \left( \frac{R_1 + R_2}{L} \right) t}, t \geq 0$$


$$\text{Total energy lost} = \int_0^{\infty} \frac{v^2 (R_1 + R_2)}{R_2^2} e^{-2 \left( \frac{R_1 + R_2}{L} \right) t} dt = \frac{v^2 (R_1 + R_2)}{R_2^2} \left[ \frac{e^{-2 \left( \frac{R_1 + R_2}{L} \right) t}}{-2 \left( \frac{R_1 + R_2}{L} \right)} \right]_0^{\infty} = \frac{Lv^2}{2R_2^2}$$

From the conservation of energy, this must also be equal to the decrease in energy stored by the inductor:

$$\text{Decrease in energy stored by inductor} = \frac{Li^2(0)}{2} - \frac{Li^2(\infty)}{2} = \frac{Lv^2}{2R_2^2}$$


Q.4

Time  $t < 0$

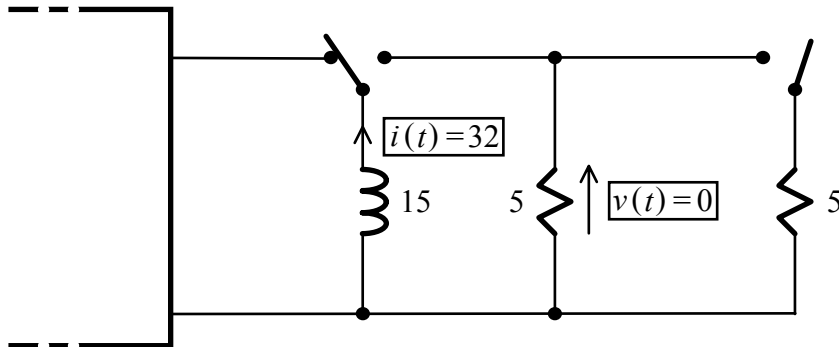


Time  $t = 0$  just after the first switch is activated

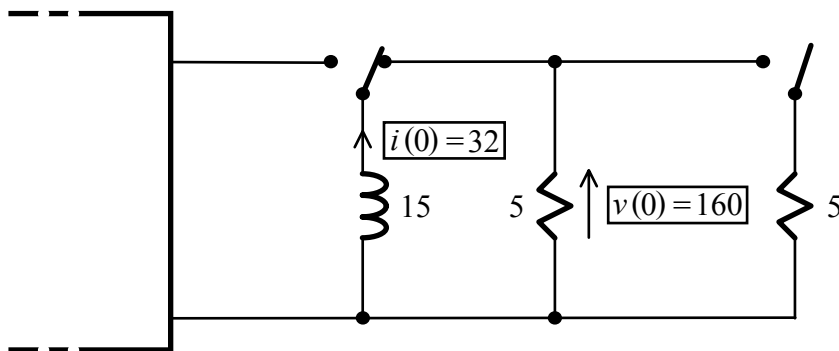Since the current in the inductor must be continuous, the inductor must be carrying the same 32A of current just after the first switch is activated:



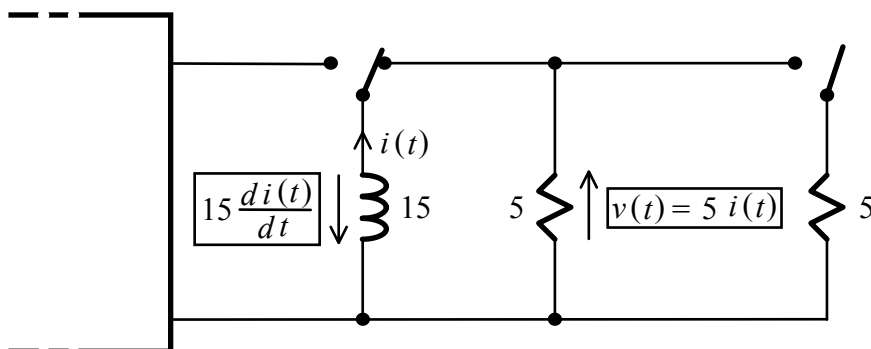Time  $t \geq 0$  and  $t < 3$  after activating 1st switch but before closing 2nd switch



$$15 \frac{di(t)}{dt} + 5i(t) = 0 \Rightarrow \frac{di(t)}{dt} + \frac{i(t)}{3} = 0 \Rightarrow i(t) = ke^{-\frac{t}{3}}, 0 \leq t < 3$$


$$i(0) = k = 32 \Rightarrow i(t) = 32e^{-\frac{t}{3}}, 0 \leq t < 3$$

$$v(t) = 5i(t) = 160e^{-\frac{t}{3}}, 0 \leq t < 3$$




*Time  $t = 3$  just after closing second switch*

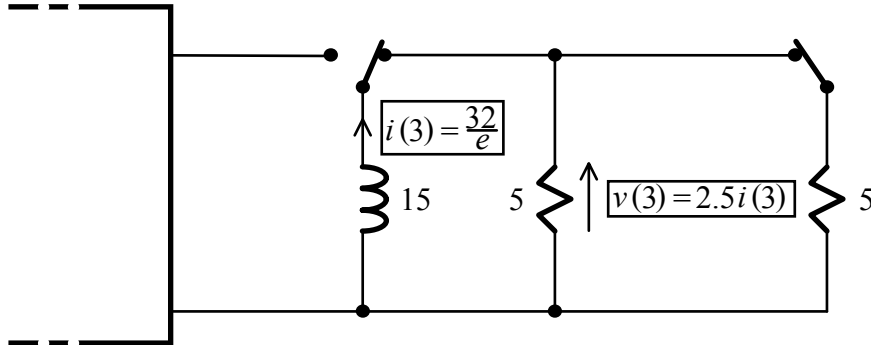Since the current in the inductor must be continuous,  $i(t)$  must be the same as  $32e^{-3/3} = 32e^{-1}$  A just before closing this switch:



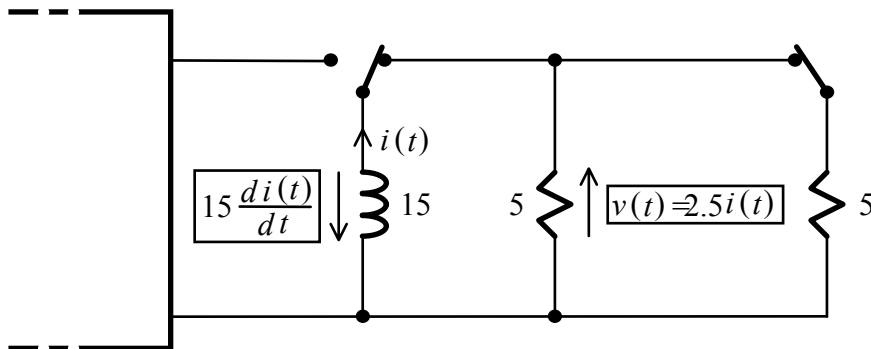*Time  $t \geq 3$  after closing second switch*



$$15 \frac{di(t)}{dt} + 2.5i(t) = 0 \Rightarrow \frac{di(t)}{dt} + \frac{i(t)}{6} = 0 \Rightarrow i(t) = he^{-\frac{t}{6}}, 3 \leq t$$

$$i(3) = he^{-\frac{3}{6}} = 32e^{-1} \Rightarrow h = 32e^{\frac{1}{2}} \Rightarrow i(t) = 32e^{-1} e^{-\frac{(t-3)}{6}}, 3 \leq t$$

$$v(t) = 2.5i(t) = 80e^{-1} e^{-\frac{(t-3)}{6}}, 3 \leq t$$

*Voltage and current waveforms*

